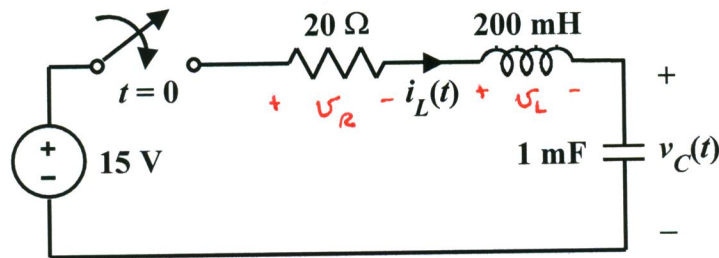


EE 2240
Problem #04

Find $v_C(t)$ for $t > 0$ if $v_C(0) = 0$ V and $i_L(0) = 0$.



$$i_L(t) = (1\text{mF}) \dot{v}_C \Rightarrow \dot{v}_C = 1000 i_L \Rightarrow \dot{v}_C(0) = 1000 i_L(0) = 0$$

$$v_R = (20\Omega) i_L = 0.02 \dot{v}_C$$

$$v_L = (200\text{mH}) \frac{di_L}{dt} = 0.0002 \ddot{v}_C$$

$$v_L + v_R + v_C = 0 \Rightarrow 0.0002 \ddot{v}_C + 0.02 \dot{v}_C + v_C = 0$$

$$\therefore \ddot{v}_C + 100 \dot{v}_C + 5000 v_C = 0$$

$$r^2 + 100r + 5000 = (r + 50)^2 + (50)^2$$

$$\Rightarrow r = -50 \pm j50$$

$$v_C(t) = e^{-50t} (K_1 \cos 50t + K_2 \sin 50t) + K_3$$

$$v_C(\infty) = 15\text{V} \Rightarrow K_3 = 15$$

$$\therefore v_C(t) = e^{-50t} (K_1 \cos 50t + K_2 \sin 50t) + 15$$

$$\dot{v}_C(t) = -50 e^{-50t} (K_1 \cos 50t + K_2 \sin 50t) + e^{-50t} (-50 K_1 \sin 50t + 50 K_2 \cos 50t)$$

$$v_C(0) = K_1 + 15 = 0 \quad \left\{ \begin{array}{l} K_1 = -15 \\ K_2 = K_1 = -15 \end{array} \right.$$

$$\dot{v}_C(0) = -50K_1 + 50K_2 = 0$$

$$\therefore v_C(t) = e^{-50t} (-15 \cos 50t - 15 \sin 50t) + 15$$

$$= 15 \left[1 - e^{-50t} (\cos 50t + \sin 50t) \right] \quad \text{V, } t \geq 0$$