

EE 2240
Problem #06

Determine the value of V_x .

