

EE 2240  
Problem #07

Determine the value of  $V_x$ .

