

EE 2240
Problem #09

Determine the value of I_o .

