
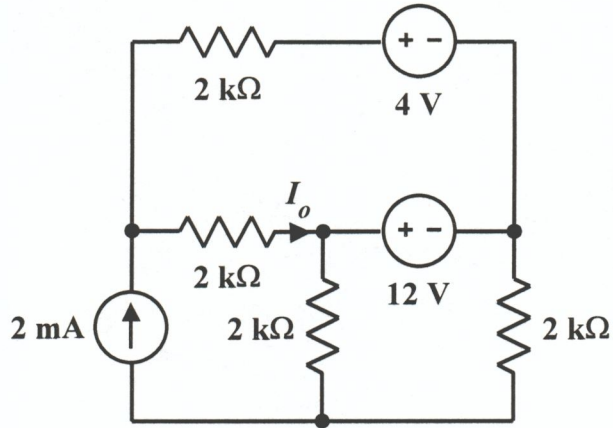


EE 2240  
**Problem #02**

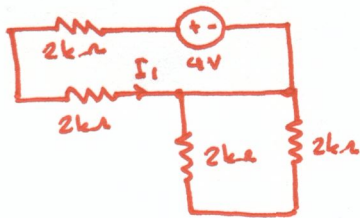Use superposition to find  $I_o$ . Show the details of your work.




For the 4V source:




$$I_1 = \frac{4V}{2k\Omega + 2k\Omega} = 1mA$$

For the 12V source:

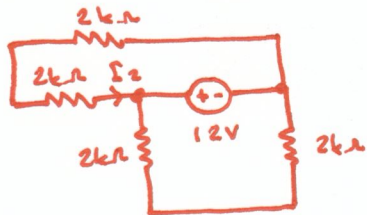

$$I_2 = - \frac{12V}{2k\Omega + 2k\Omega} = -3mA$$

For the 2mA source:

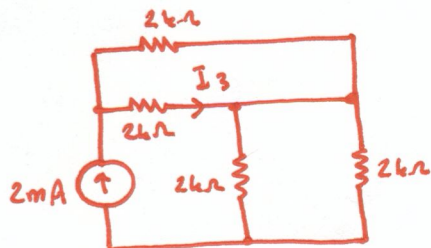

$$I_3 = \frac{2k\Omega}{2k\Omega + 2k\Omega} (2mA) = 1mA$$

$$I_o = I_1 + I_2 + I_3 = 1 - 3 + 1 = -1mA$$