

EE 2240  
**Problem #03**

Find  $V_o$  using superposition. Show the details of your work.

