

EE 2240
Problem #02

Treat the $4\ \Omega$ resistor as the load, and use Thévenin's theorem to find V_o .

