

For Example 2 :

V1	1	0	10
R1	1	2	1000
R2	2	0	3000

$$v_2 = \frac{3}{4} \times 10 = 7.5 \text{ V}$$

$$i_{V1} = -2.5 \text{ mA}$$

