
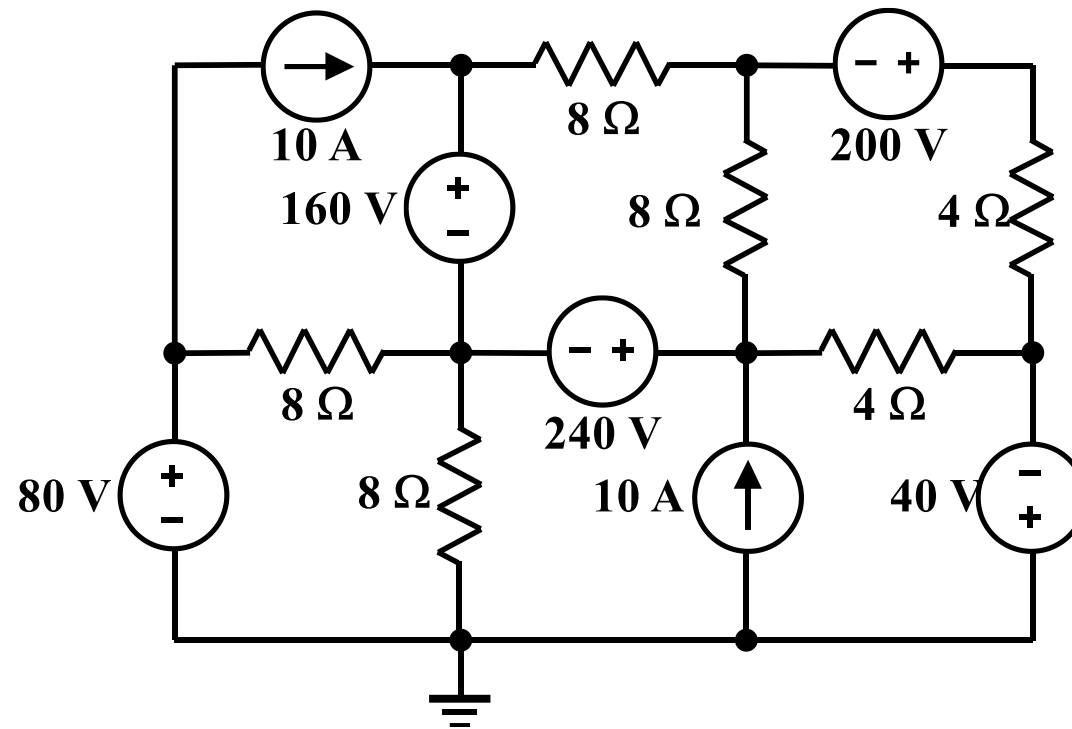


## *A Detailed Modified Nodal Analysis Example*


Given the circuit shown:

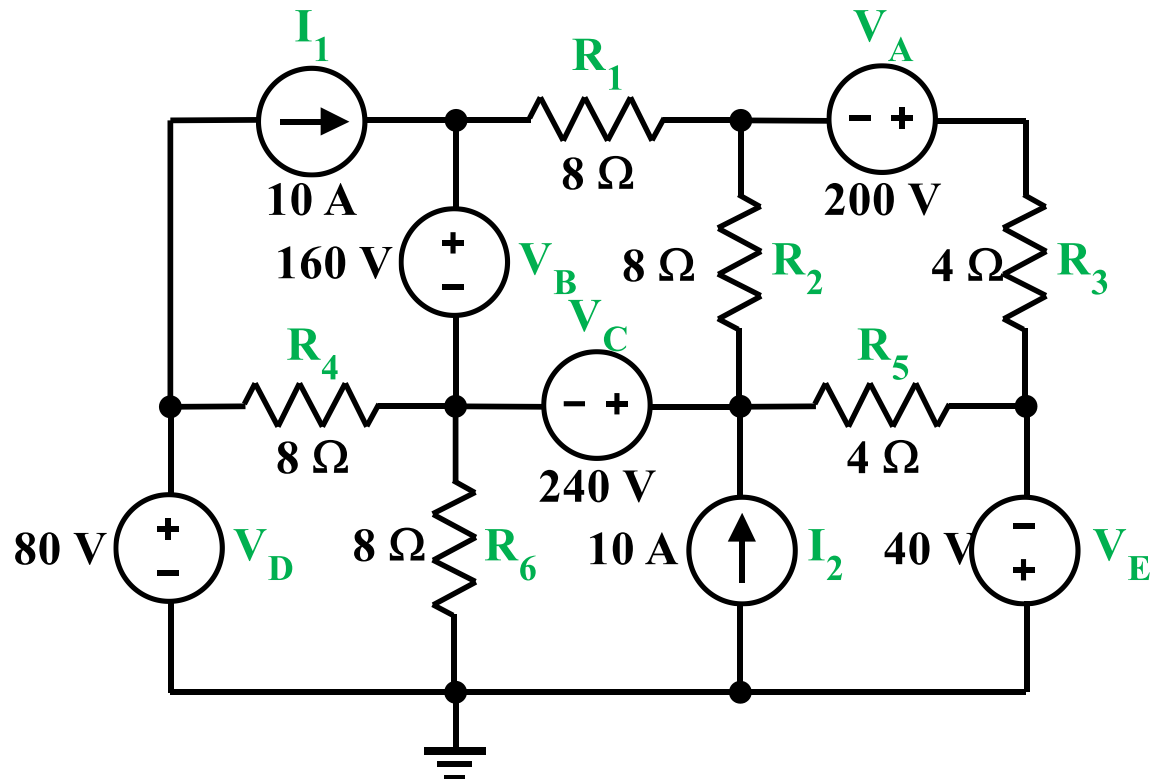


Label the components (shown here in green):



Label the nodes (shown here in red):

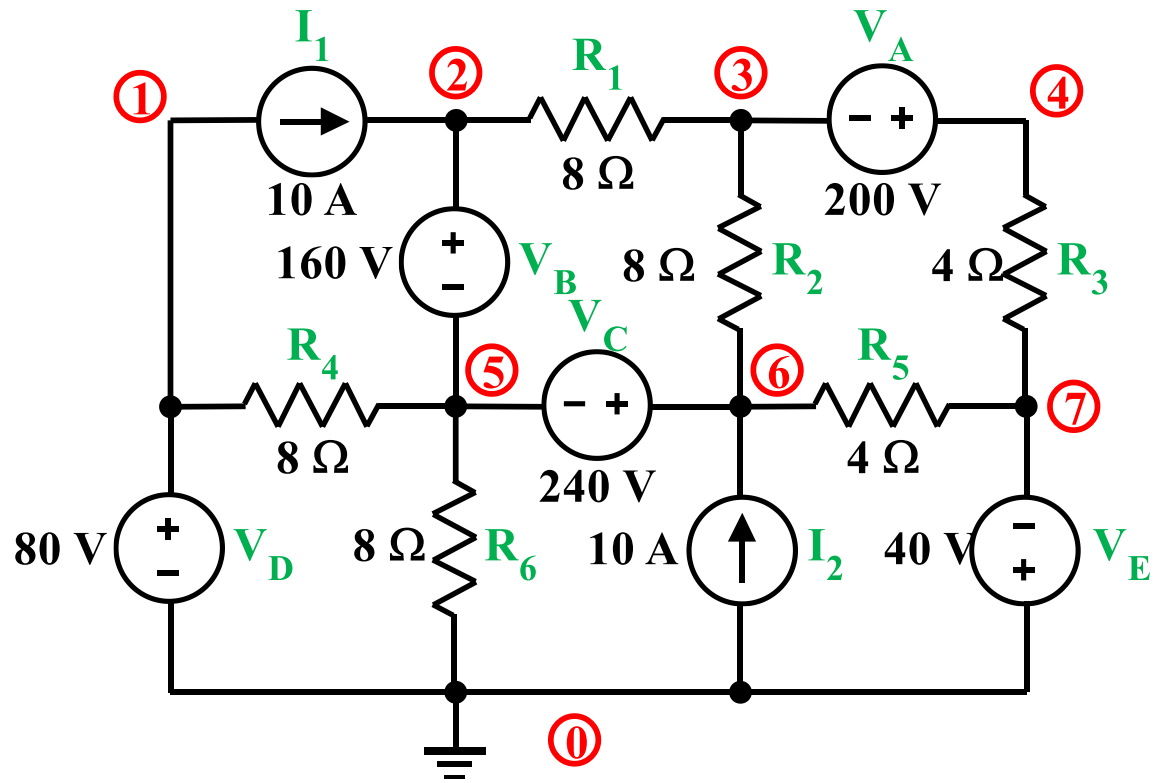

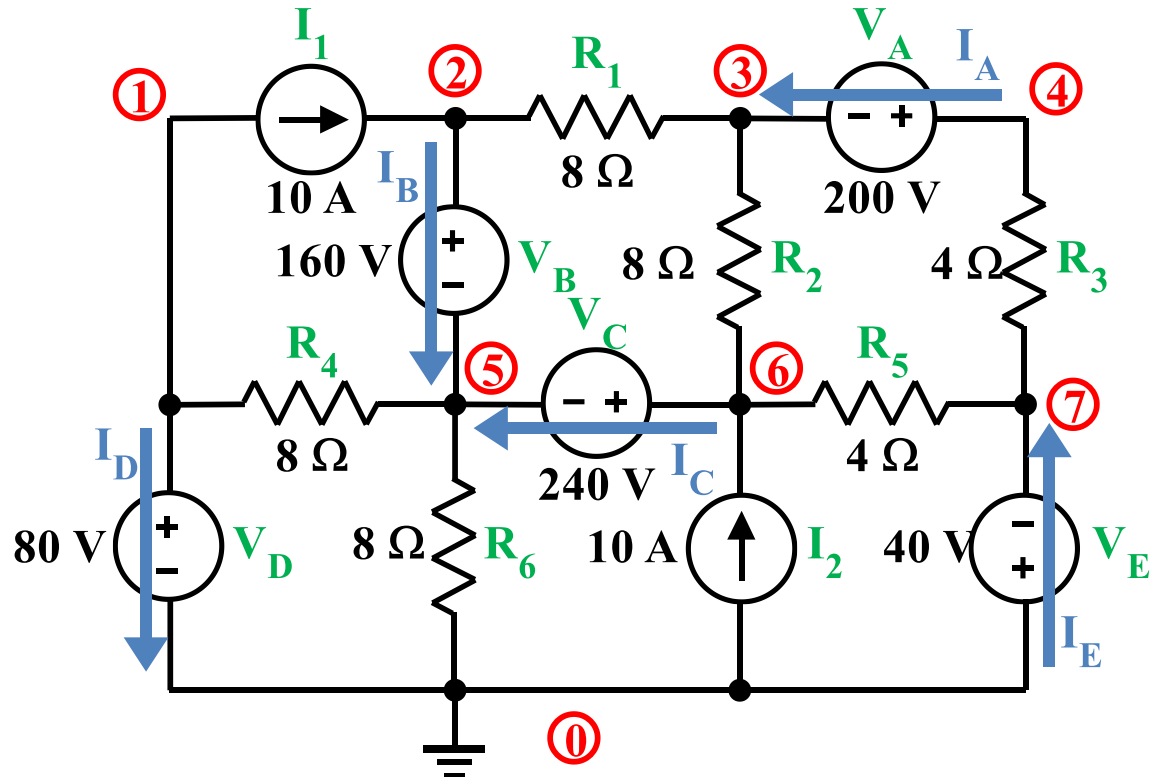Define a current through each independent voltage source (must satisfy the Passive Sign Convention, **shown here in blue**).



Write a KCL equation at each node (except the reference node), with independent current sources on the right-hand side. Currents leaving the node are taken as positive.

$$\text{Node 1: } \frac{V_1 - V_5}{R_4} + I_D = -I_1$$

$$\text{Node 2: } \frac{V_2 - V_3}{R_1} + I_B = I_1$$

$$\text{Node 3: } \frac{V_3 - V_2}{R_1} + \frac{V_3 - V_6}{R_2} - I_A = 0$$

$$\text{Node 4: } I_A + \frac{V_4 - V_7}{R_3} = 0$$

$$\text{Node 5: } -I_B + \frac{V_5 - V_1}{R_4} + \frac{V_5}{R_6} - I_C = 0$$

$$\text{Node 6: } I_C + \frac{V_6 - V_3}{R_2} + \frac{V_6 - V_7}{R_5} = I_2$$

$$\text{Node 7: } \frac{V_7 - V_4}{R_3} + \frac{V_7 - V_6}{R_5} - I_E = 0$$

$$\text{Node 0: } -I_D - \frac{V_5}{R_6} + I_E = -I_2$$

This equation is redundant and as noted above, by convention, is normally not included

We will ignore it in the following discussion.

Write a constraint equation for each voltage source, with independent voltage sources on the right-hand side:

$$V_A: \quad V_4 - V_3 = V_A$$

$$V_B: \quad V_2 - V_5 = V_B$$

$$V_C: \quad V_6 - V_5 = V_C$$

$$V_D: \quad V_1 = V_D$$

$$V_E: \quad -V_7 = V_E$$

Express *all* equations in the combined matrix form shown below. (Blank spaces are zeros, not shown for easier visualization.)

		Node Voltages							Voltage-Source Currents						
		$V_1$	$V_2$	$V_3$	$V_4$	$V_5$	$V_6$	$V_7$	$I_A$	$I_B$	$I_C$	$I_D$	$I_E$		
Node Numbers	$N_1$	$\frac{1}{R_4}$				$-\frac{1}{R_4}$						1		$V_1$	$-I_1$
	$N_2$		$\frac{1}{R_1}$	$-\frac{1}{R_1}$						1				$V_2$	$I_1$
	$N_3$		$-\frac{1}{R_1}$	$\frac{1}{R_1} + \frac{1}{R_2}$			$-\frac{1}{R_2}$		-1					$V_3$	0
	$N_4$				$\frac{1}{R_3}$			$-\frac{1}{R_3}$	1					$V_4$	0
	$N_5$	$-\frac{1}{R_4}$				$\frac{1}{R_4} + \frac{1}{R_6}$				-1	-1			$V_5$	0
	$N_6$			$-\frac{1}{R_2}$			$\frac{1}{R_2} + \frac{1}{R_5}$	$-\frac{1}{R_5}$			1			$V_6$	$I_2$
	$N_7$				$-\frac{1}{R_3}$		$-\frac{1}{R_5}$	$\frac{1}{R_3} + \frac{1}{R_5}$					-1	$V_7$	0
Voltage Sources	$V_A$			-1	1									$I_A$	$V_A$
	$V_B$		1			-1								$I_B$	$V_B$
	$V_C$					-1	1							$I_C$	$V_C$
	$V_D$	1												$I_D$	$V_D$
	$V_E$							-1						$I_E$	$V_E$

$\times$

$=$

Alternatively, to do this analysis with SCAM:

Create a SPICE-like netlist file called "My\_Example.cir" and save it in the MATLAB path. (Note that there is no title line, no .end line, and no analysis command.)

```
I1 1 2 10
R1 2 3 8
VA 4 3 200
VB 2 5 160
R2 3 6 8
R3 4 7 4
R4 1 5 8
VC 6 5 240
R5 6 7 4
VD 1 0 80
R6 5 0 8
I2 0 6 10
VE 0 7 40
```

Then, in MATLAB do the following:

```
>> fname="My_Example.cir";
>> ISU_scam
```

Started -- please be patient.

```
Netlist:
I1 1 2 10
R1 2 3 8
VA 4 3 200
VB 2 5 160
R2 3 6 8
R3 4 7 4
R4 1 5 8
VC 6 5 240
R5 6 7 4
```



VD 1 0 80  
 R6 5 0 8  
 I2 0 6 10  
 VE 0 7 40

The A matrix:

$$\begin{bmatrix}
 1/R4, & 0, & 0, & 0, & -1/R4, & 0, & 0, & 0, & 0, & 0, & 1, & 0 \\
 0, & 1/R1, & -1/R1, & 0, & 0, & 0, & 0, & 0, & 1, & 0, & 0, & 0 \\
 0, & -1/R1, & 1/R1 + 1/R2, & 0, & 0, & -1/R2, & 0, & -1, & 0, & 0, & 0, & 0 \\
 0, & 0, & 0, & 1/R3, & 0, & 0, & -1/R3, & 1, & 0, & 0, & 0, & 0 \\
 -1/R4, & 0, & 0, & 0, & 1/R4 + 1/R6, & 0, & 0, & 0, & -1, & -1, & 0, & 0 \\
 0, & 0, & -1/R2, & 0, & 0, & 1/R2 + 1/R5, & -1/R5, & 0, & 0, & 1, & 0, & 0 \\
 0, & 0, & 0, & -1/R3, & 0, & -1/R5, & 1/R3 + 1/R5, & 0, & 0, & 0, & 0, & -1 \\
 0, & 0, & -1, & 1, & 0, & 0, & 0, & 0, & 0, & 0, & 0, & 0 \\
 0, & 1, & 0, & 0, & -1, & 0, & 0, & 0, & 0, & 0, & 0, & 0 \\
 0, & 0, & 0, & 0, & -1, & 1, & 0, & 0, & 0, & 0, & 0, & 0 \\
 1, & 0, & 0, & 0, & 0, & 0, & 0, & 0, & 0, & 0, & 0, & 0 \\
 0, & 0, & 0, & 0, & 0, & 0, & -1, & 0, & 0, & 0, & 0, & 0
 \end{bmatrix}$$

The x vector:

v\_1  
 v\_2  
 v\_3  
 v\_4  
 v\_5  
 v\_6  
 v\_7  
 I\_VA  
 I\_VB  
 I\_VC  
 I\_VD  
 I\_VE

The z vector:

-I1

I1  
0  
0  
0  
I2  
0  
VA  
VB  
VC  
VD  
VE

The matrix equation:

$$\begin{aligned}
 I_{VD} + v_1/R4 - v_5/R4 &== -I1 \\
 I_{VB} + v_2/R1 - v_3/R1 &== I1 \\
 v_3*(1/R1 + 1/R2) - v_2/R1 - v_6/R2 - I_{VA} &== 0 \\
 I_{VA} + v_4/R3 - v_7/R3 &== 0 \\
 v_5*(1/R4 + 1/R6) - I_{VC} - v_1/R4 - I_{VB} &== 0 \\
 I_{VC} - v_3/R2 - v_7/R5 + v_6*(1/R2 + 1/R5) &== I2 \\
 v_7*(1/R3 + 1/R5) - v_4/R3 - v_6/R5 - I_{VE} &== 0 \\
 v_4 - v_3 &== VA \\
 v_2 - v_5 &== VB \\
 v_6 - v_5 &== VC \\
 v_1 &== VD \\
 -v_7 &== VE
 \end{aligned}$$

The solution:

$$v_1 == VD$$

$$\begin{aligned}
 v_2 == & (R1*R2*R4*R5*VB - R2*R4*R5*R6*VA - R1*R4*R5*R6*VA + R1*R2*R4*R6*VB + R1*R3*R4*R5*VB + R1*R2*R5*R6*VB \\
 & + R1*R3*R4*R6*VB + R2*R3*R4*R5*VB + R1*R3*R5*R6*VB + R2*R3*R4*R6*VB + R1*R4*R5*R6*VB + R2*R3*R5*R6*VB - \\
 & R1*R2*R4*R6*VC - R1*R3*R4*R6*VC - R2*R3*R4*R6*VC - R1*R4*R5*R6*VC + R1*R2*R5*R6*VD + R1*R3*R5*R6*VD + \\
 & R2*R3*R5*R6*VD - R1*R2*R4*R6*VE - R1*R3*R4*R6*VE - R2*R3*R4*R6*VE - R1*R4*R5*R6*VE - R2*R4*R5*R6*VE + \\
 & I1*R1*R2*R4*R5*R6 + I1*R1*R3*R4*R5*R6 + I2*R1*R2*R4*R5*R6 + I1*R2*R3*R4*R5*R6 + I2*R1*R3*R4*R5*R6 + \\
 & I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 + \\
 & R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)
 \end{aligned}$$

$$v_3 == -(R1*R2*R4*R5*VA + R1*R2*R4*R6*VA + R1*R2*R5*R6*VA + R1*R4*R5*R6*VA + R2*R4*R5*R6*VA - R2*R3*R4*R5*VB - R2*R3*R4*R6*VB - R2*R3*R5*R6*VB - R1*R3*R4*R5*VC - R1*R3*R5*R6*VC + R2*R3*R4*R6*VC - R1*R3*R5*R6*VD - R2*R3*R5*R6*VD + R1*R2*R4*R5*VE + R1*R2*R4*R6*VE + R1*R2*R5*R6*VE + R1*R3*R4*R6*VE + R2*R3*R4*R6*VE + R1*R4*R5*R6*VE + R2*R4*R5*R6*VE - I1*R1*R3*R4*R5*R6 - I1*R2*R3*R4*R5*R6 - I2*R1*R3*R4*R5*R6 - I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)$$

$$v_4 == (R1*R3*R4*R5*VA + R1*R3*R4*R6*VA + R2*R3*R4*R5*VA + R1*R3*R5*R6*VA + R2*R3*R4*R6*VA + R2*R3*R5*R6*VA + R2*R3*R4*R5*VB + R2*R3*R4*R6*VB + R2*R3*R5*R6*VB + R1*R3*R4*R5*VC + R1*R3*R5*R6*VC - R2*R3*R4*R6*VC + R1*R3*R5*R6*VD + R2*R3*R5*R6*VD - R1*R2*R4*R5*VE - R1*R2*R4*R6*VE - R1*R2*R5*R6*VE - R1*R3*R4*R6*VE - R2*R3*R4*R6*VE - R1*R4*R5*R6*VE - R2*R4*R5*R6*VE + I1*R1*R3*R4*R5*R6 + I1*R2*R3*R4*R5*R6 + I2*R1*R3*R4*R5*R6 + I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)$$

$$v_5 == -(R6*(R1*R4*R5*VA + R2*R4*R5*VA + R2*R4*R5*VB + R1*R2*R4*VC + R1*R3*R4*VC + R2*R3*R4*VC + R1*R4*R5*VC - R1*R2*R5*VD - R1*R3*R5*VD - R2*R3*R5*VD + R1*R2*R4*VE + R1*R3*R4*VE + R2*R3*R4*VE + R1*R4*R5*VE + R2*R4*R5*VE - I1*R1*R2*R4*R5 - I1*R1*R3*R4*R5 - I2*R1*R2*R4*R5 - I1*R2*R3*R4*R5 - I2*R1*R3*R4*R5 - I2*R2*R3*R4*R5))/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)$$

$$v_6 == (R1*R2*R4*R5*VC - R2*R4*R5*R6*VA - R2*R4*R5*R6*VB - R1*R4*R5*R6*VA + R1*R3*R4*R5*VC + R1*R2*R5*R6*VC + R2*R3*R4*R5*VC + R1*R3*R5*R6*VC + R2*R3*R5*R6*VC + R2*R4*R5*R6*VC + R1*R2*R5*R6*VD + R1*R3*R5*R6*VD + R2*R3*R5*R6*VD - R1*R2*R4*R6*VE - R1*R3*R4*R6*VE - R2*R3*R4*R6*VE - R1*R4*R5*R6*VE - R2*R4*R5*R6*VE + I1*R1*R2*R4*R5*R6 + I1*R1*R3*R4*R5*R6 + I2*R1*R2*R4*R5*R6 + I1*R2*R3*R4*R5*R6 + I2*R1*R3*R4*R5*R6 + I2*R2*R3*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)$$

$$v_7 == -VE$$

$$I\_VA == -(R1*R4*R5*VA + R1*R4*R6*VA + R2*R4*R5*VA + R1*R5*R6*VA + R2*R4*R6*VA + R2*R5*R6*VA + R2*R4*R5*VB + R2*R4*R6*VB + R2*R5*R6*VB + R1*R4*R5*VC + R1*R5*R6*VC - R2*R4*R6*VC + R1*R5*R6*VD + R2*R5*R6*VD + R1*R4*R5*VE + R2*R4*R5*VE + R1*R5*R6*VE + R2*R5*R6*VE + I1*R1*R4*R5*R6 + I1*R2*R4*R5*R6 + I2*R1*R4*R5*R6 + I2*R2*R4*R5*R6)/(R1*R2*R4*R5 + R1*R2*R4*R6 + R1*R3*R4*R5 + R1*R2*R5*R6 + R1*R3*R4*R6 + R2*R3*R4*R5 + R1*R3*R5*R6 + R2*R3*R4*R6 + R1*R4*R5*R6 + R2*R3*R5*R6 + R2*R4*R5*R6)$$

$$I\_VB == (R2*R4*R6*VC - R2*R4*R6*VA - R2*R5*R6*VA - R2*R4*R5*VB - R2*R4*R6*VB - R3*R4*R5*VB - R2*R5*R6*VB -$$



```
>> eval(z)
```

```
ans =
```

```
-10  
10  
0  
0  
0  
10  
0  
200  
160  
240  
80  
40
```

```
or
```

```
>> eval(I_VC)
```

```
ans =
```

```
-45
```