

EE 3340

Homework Problem #008

Construct a phasor diagram showing the relative magnitudes and phase angles of \mathbf{I}_R , \mathbf{I}_L , \mathbf{I}_C , and \mathbf{I}_T . A sheet of polar graph paper is attached.



