

Homework Problem #009

For the circuit shown below, use the phasor analysis method to determine the AC steady-state part of $v_1(t)$, $v_2(t)$, $i_L(t)$, $i_R(t)$ and $i_C(t)$. Express your answers in polar form with the phase angles in degrees.

