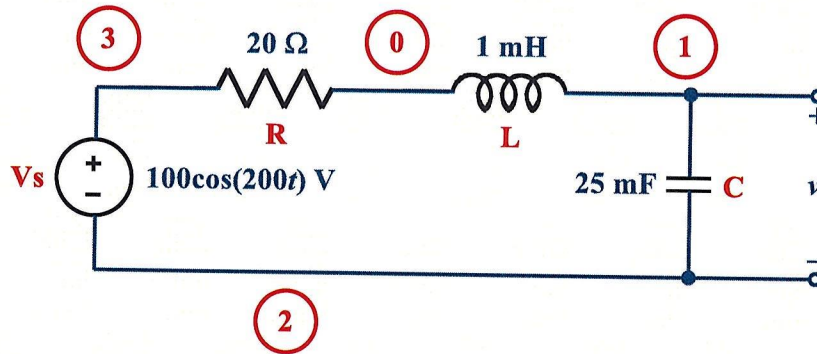


Homework Problem #013

- a. For the circuit shown below:



the following LTspice netlist can be used to determine the magnitude and phase angle of the steady-state AC part of v :

```
Vs 3 2 AC 100 0
R 3 0 20
L 0 1 1m
C 1 2 25m
.AC DEC 1 31.83098861 31.83098861
```

Run the simulation and identify the desired results in the output file.

See the attached page.

- b. Use the phasor analysis method to determine the analytical solution, and verify that the LTspice result is correct.

$$\begin{aligned}
 V &= \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} & V_s &= \frac{V_s}{1 - \omega^2 LC + j\omega RC} \\
 &= \frac{100 \angle 0^\circ}{[1 - (200)^2 (0.001)(0.025)] + j(200)(20)(0.025)} \\
 &= \frac{100 \angle 0^\circ}{j100} \\
 &= 1 \angle -90^\circ \text{ V}
 \end{aligned}$$

```
* Q:\Websites\RES\EE 3340\homework problems\Spring 2022 EE 3340 Homework Problem 13.cir
Vs 3 2 AC 100 0
R 3 0 20
L 0 1 1m
C 1 2 25m
.AC DEC 1 31.83098861 31.83098861
.end
```

--- AC Analysis ---

frequency:	31.831	Hz		
V(3):	mag: 99.995	phase: 3.01631e-010°	voltage	
V(2):	mag: 0.00499975	phase: 180°	voltage	
V(1):	mag: 0.999963	phase: -90.2865°	voltage	
I(C):	mag: 4.99975	phase: 3.01631e-010°	device_current	
I(L):	mag: 4.99975	phase: 3.01631e-010°	device_current	
I(R):	mag: 4.99975	phase: 3.01631e-010°	device_current	
I(Vs):	mag: 4.99975	phase: -180°	device_current	

$$V \approx 1 \angle -90^\circ \quad V$$