

EE 3340

**Homework Problem #018**

Use phasor analysis to determine the steady-state AC part of  $v_R$ . Express your result in the time domain, with the phase angle expressed in degrees.

