

EE 3340

**Homework Problem #020**

What value of  $\omega$  will cause the steady-state AC part of  $v_o$  to be zero?

