

EE 3340

Homework Problem #030

Symbolically determine the input impedance of the circuit shown below.

