

EE 3340

Homework Problem #032

Use LTspice to determine the input impedance of the circuit shown below in polar form at $\omega = 120\pi$ rad/s. Show your work.

