

EE 3340  
**Homework Problem #034**

Determine the voltage transfer function  $V_2/V_1$ . Show your work.

