

Homework Problem #036

Determine the phasor values of the mesh currents I_1 and I_2 (in polar form) in the circuit shown below. Show your work.

