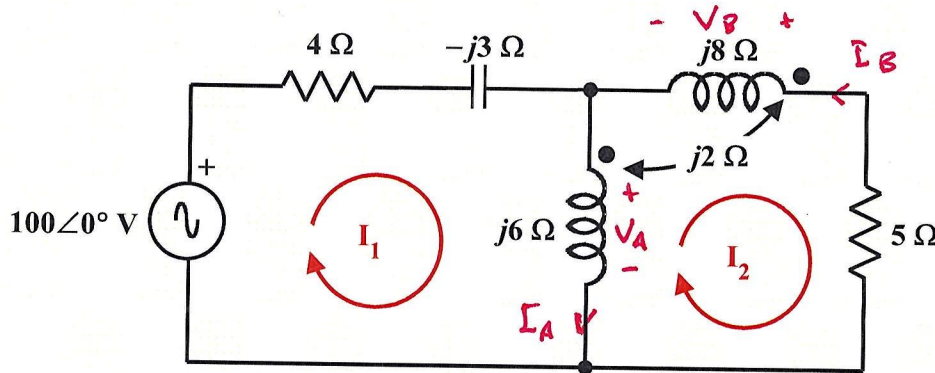


## Homework Problem #036

Determine the phasor values of the mesh currents  $I_1$  and  $I_2$  (in polar form) in the circuit shown below. Show your work.



$$V_A = j6 I_A + j2 I_B$$

$$V_B = j8 I_B + j2 I_A$$

$$\text{But } I_A = I_1 - I_2 \text{ and } I_B = -I_2$$

$$\begin{aligned} \therefore V_A &= j6 (I_1 - I_2) + j2 (-I_2) \\ &= j6 I_1 - j8 I_2 \end{aligned}$$

$$\begin{aligned} V_B &= j8 (-I_2) + j2 (I_1 - I_2) \\ &= j2 I_1 - j10 I_2 \end{aligned}$$

KCL for mesh 1:

$$(4 - j3) I_1 + V_A = 100$$

$$\Rightarrow (4 - j3) I_1 + j6 I_1 - j8 I_2 = 100$$

$$\text{or } (4 + j3) I_1 - j8 I_2 = 100$$

KCL for mesh 2:

$$-V_A - V_B + 5 I_2 = 0$$

$$\Rightarrow -j6 I_1 + j8 I_2 - j2 I_1 + j10 I_2 + 5 I_2 = 0$$

$$\text{or } -j8 I_1 + (5 + j18) I_2 = 0$$

In matrix form:

$$\underbrace{\begin{bmatrix} 4+j3 & -j8 \\ -j8 & 5+j18 \end{bmatrix}}_A \underbrace{\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}}_b = \underbrace{\begin{bmatrix} 100 \\ 0 \end{bmatrix}}_c$$

Solving with MATLAB:

(See attached page.)

$$I_1 \approx 20.30 \angle 3.50^\circ \text{ A}$$

$$I_2 \approx 8.69 \angle 19.03^\circ \text{ A}$$

```
>> A=[4+j*3 -j*8; -j*8 5+j*18]
```

```
A =
```

```
4.0000 + 3.0000i 0.0000 - 8.0000i  
0.0000 - 8.0000i 5.0000 +18.0000i
```

```
>> c=[100; 0]
```

```
c =
```

```
100  
0
```

```
>> b=A\c
```

```
b =
```

```
20.2621 + 1.2398i  
8.2182 + 2.8339i
```

```
>> I1_magnitude=abs(b(1))
```

```
I1_magnitude =
```

```
20.3000
```

←  $|I_1|$

```
>> I1_phase_rad=angle(b(1))
```

```
I1_phase_rad =
```

```
0.0611
```

←  $\angle I_1$  in radians

```
>> I1_phase_deg=angle(b(1))*180/pi
```

```
I1_phase_deg =
```

```
3.5015
```

←  $\angle I_1$  in degrees

```
>> I2_magnitude=abs(b(2))
```

```
I2_magnitude =
```

```
8.6931
```

←  $|I_2|$

```
>> I2_phase_rad=angle(b(2))
```

```
I2_phase_rad =
```

```
0.3321
```

←  $\angle I_2$  in radians

```
>> I2_phase_deg=angle(b(2))*180/pi
```

```
I2_phase_deg =
```

```
19.0256
```

←  $\angle I_2$  in degrees