

Homework Problem #040

For the circuit shown below, calculate the phase currents (\mathbf{I}_{AB} , \mathbf{I}_{BC} and \mathbf{I}_{CA}) and the line currents (\mathbf{I}_{aA} , \mathbf{I}_{bB} and \mathbf{I}_{cC}) in polar form with angles in degrees.

