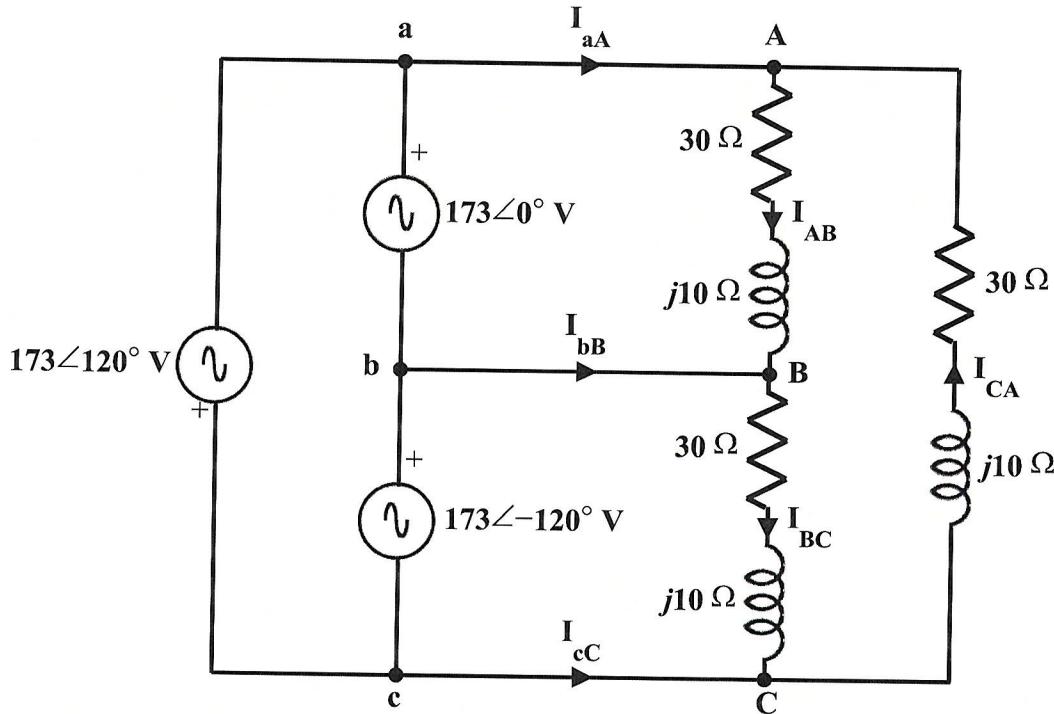


EE 3340  
Homework Problem #040

For the circuit shown below, calculate the phase currents ( $I_{AB}$ ,  $I_{BC}$  and  $I_{CA}$ ) and the line currents ( $I_{aA}$ ,  $I_{bB}$  and  $I_{cC}$ ) in polar form with angles in degrees.



$$\text{Let } Z_\Delta = 30 + j10 \approx 31.62 \angle 18.43^\circ \Omega$$

The phase currents are:

$$I_{AB} = \frac{V_{ab}}{Z_\Delta} = \frac{173 \angle 0^\circ}{31.62 \angle 18.43^\circ} \approx 5.47 \angle -18.43^\circ \text{ A}$$

$$I_{BC} = \frac{V_{bc}}{Z_\Delta} \approx 5.47 \angle -138.43^\circ \text{ A}$$

$$I_{CA} = \frac{V_{ca}}{Z_\Delta} \approx 5.47 \angle 101.57^\circ \text{ A}$$

The line currents are:

$$I_{aA} = I_{AB} - I_{CA} \approx 9.48 \angle -48.43^\circ \text{ A}$$

$$I_{bB} = I_{BC} - I_{AB} \approx 9.48 \angle -168.43^\circ \text{ A}$$

$$I_{cC} = I_{CA} - I_{BC} \approx 9.48 \angle 71.57^\circ \text{ A}$$