

Homework Problem #041

Use LTspice to verify your answers for Homework Problem #040. The circuit schematic diagram is reproduced below.

