

Homework Problem #043

Find the line currents, I_{aA} , I_{bB} and I_{cC} (in polar form) in the unbalanced three-phase circuit shown below.

