

EE 3340
Homework Problem #045


In response to an input signal voltage

$$v_s(t) = 24 \cos 2000\pi t \text{ V},$$

the input current in the circuit shown was measured as

$$i(t) = 6 \cos(2000\pi t - 60^\circ) \text{ mA}.$$

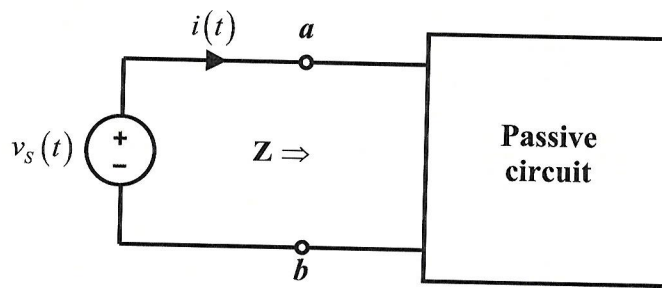Determine the equivalent input impedance Z of the circuit.



$$V_s = 24 \angle 0^\circ \text{ V}$$

$$I = 6 \angle -60^\circ \text{ A}$$

$$Z = \frac{V_s}{I} = \frac{24 \angle 0^\circ}{6 \angle -60^\circ} = 4 \angle 60^\circ \Omega$$