

EE 3340
Homework Problem #049

For the circuit shown below, determine R_{eq} .

