

# *Experiment 6:*

## *Cascaded RC Low-Pass Filters*

### **Objective**

The objective of this experiment is to explore changes to the frequency response of simple passive RC low pass filters when loaded with second and third cascaded filter sections.

### **Background**

If two passive RC low pass filters are cascaded, the frequency response is not simply the product of the two separate first-order RC transfer functions. This is because the ideal single-pole response assumes a zero-output-impedance source is driving the filter and there is no load on the output, i.e., the filter drives an infinite impedance (or open circuit). However, directly connecting the second filter acts as a load for the first effectively changing the combined RC time constant. If you try to analyze the cascaded circuit by simply adding phasors you will soon realize the shortcomings of that simple technique. This is where using circuit simulation software is very helpful.

### **Pre-Lab Exercise**

As a pre-lab exercise enter the schematic diagram shown in Figure 1 into LTspice. Three different RC low-pass filter sections are included. The inputs of all three filters are driven by the same AC source, V1. Resistor R5 and capacitor C5 form a simple single-pole (1<sup>st</sup>-order) filter with the output taken at node dB-0. Resistors R3 and R4 and capacitors C1 and C3 form a 2<sup>nd</sup>-order filter with  $R4 = R3$  and  $C3 = C1$ . Two signals from this filter should be plotted – the output of the first section at node dB-1 and the output of the second section at node dB-2. Resistors R2 and R1 and capacitors C4 and C2 form another 2<sup>nd</sup>-order filter with  $R1 = 10 \cdot R2$  and  $C2 = C4/10$ . Two similar signals from this filter should also be plotted – the output of the first section at node dB-3 and the output of the second section at node dB-4. This second filter keeps the RC time constant the same for both sections of the filter but reduces the loading effect by increasing the value of the second resistor by a factor of 10 and decreasing the value of the second capacitor by a similar factor of 10 (keeping the RC product the same). Using a factor of 10 like this is a good rule of thumb to use when designing cascaded passive RC filters.

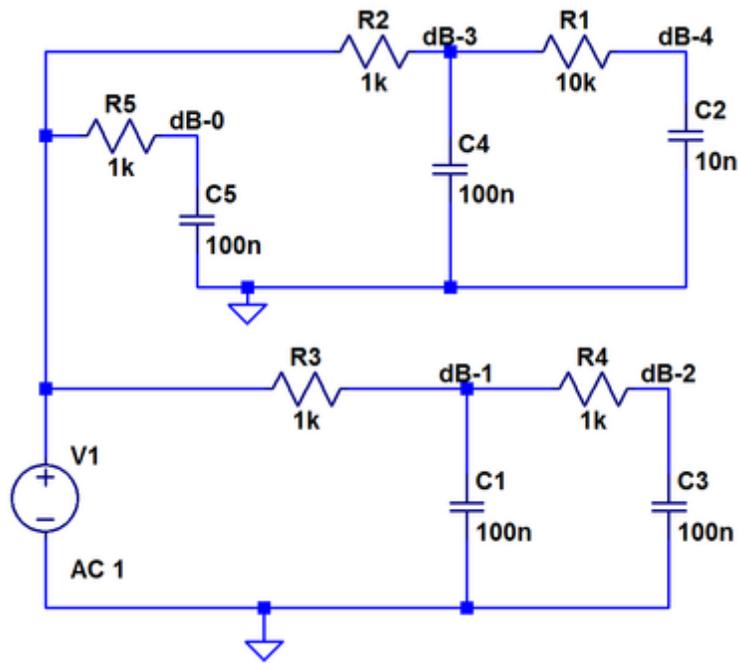


Figure 1. LTSpice Schematic Diagram of RC Filters.

Run the simulation sweeping the input frequency from 100 Hz to 20 kHz. You should get a frequency response plot that looks something like Figure 2.

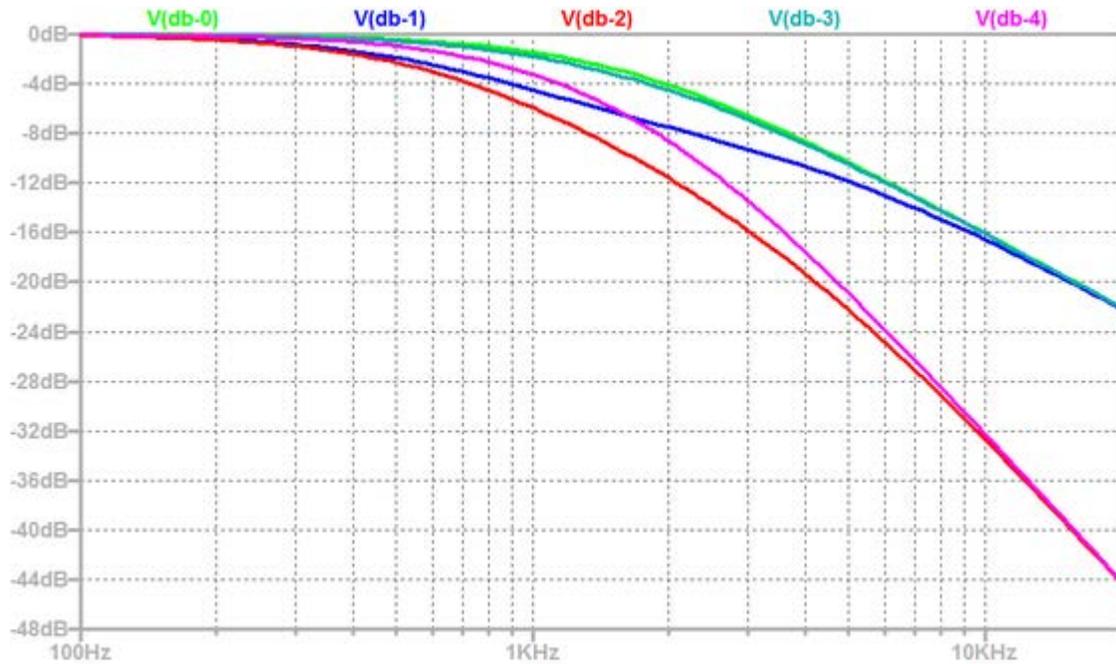


Figure 2. Plot of AC Sweep Simulation Results.

As we can see in Figure 2, the completely unloaded 1<sup>st</sup>-order filter (dB-0 green line) and the lightly-loaded 1<sup>st</sup>-order section (dB-3 slightly darker green line) are nearly on top of each other. The loaded 1<sup>st</sup>-order point (dB-1 blue line) is significantly lower than the other two lines at the frequency of the  $RC$  time constant. However, all three converge to the same line at high frequencies, 20 kHz or above. The two 2<sup>nd</sup>-order outputs at dB-2 (red line, loaded) and dB-4 (pink line, lightly loaded) also show significant differences at the  $RC$  time constant frequency but also converge to the same line at 20 kHz and above. At 20 kHz the response of the 2<sup>nd</sup>-order filters is 20 dB lower than the 1<sup>st</sup>-order filters as one would expect.

## Equipment Required

- Computer with Windows Operating System
- Fritzing Software (Optional)
- LTspice Software
- Analog Devices ADALM2000 (M2K) Advanced Active Learning Module with Scopy Software and Probe Cable
- Solderless Breadboard, and Jumper Wire Kit
- Components:
  - 3 x 1 k $\Omega$  Resistors
  - 10 k $\Omega$  Resistor
  - 100 k $\Omega$  Resistor
  - 3 x 0.1  $\mu$ F Capacitors (marked 104)
  - 0.01  $\mu$ F Capacitor (marked 103)
  - 0.001  $\mu$ F Capacitor (marked 102)

## First-Order RC Filter

### Hardware Setup

Construct the circuit shown in Figure 3 on your solderless breadboard.

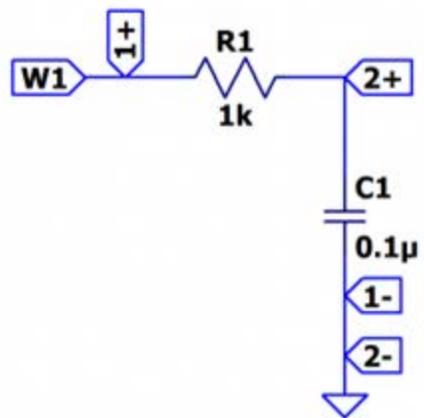


Figure 3. First-Order RC Filter.

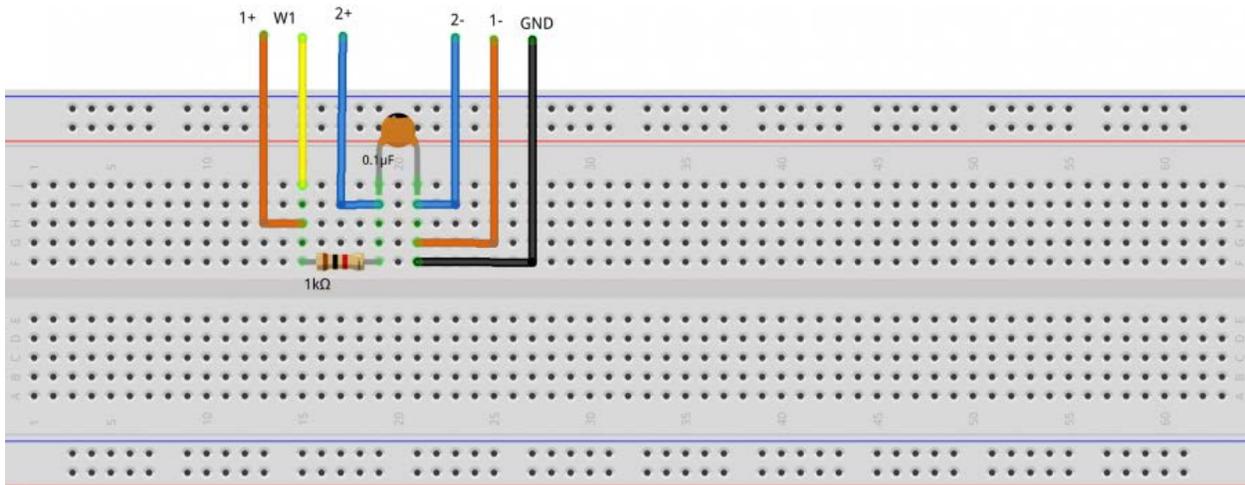


Figure 4. First-Order RC Filter Breadboard Layout.

### Procedure

With the Network Analyzer, now do a logarithmic sweep. Set the start frequency to 100 Hz and the stop frequency to 20 kHz. The magnitude axis can be set to -50 dB minimum and 10 dB maximum. The phase axis goes from -180 to 90 degrees. Run the Network Analyzer to obtain the frequency response plot of the RC filter.

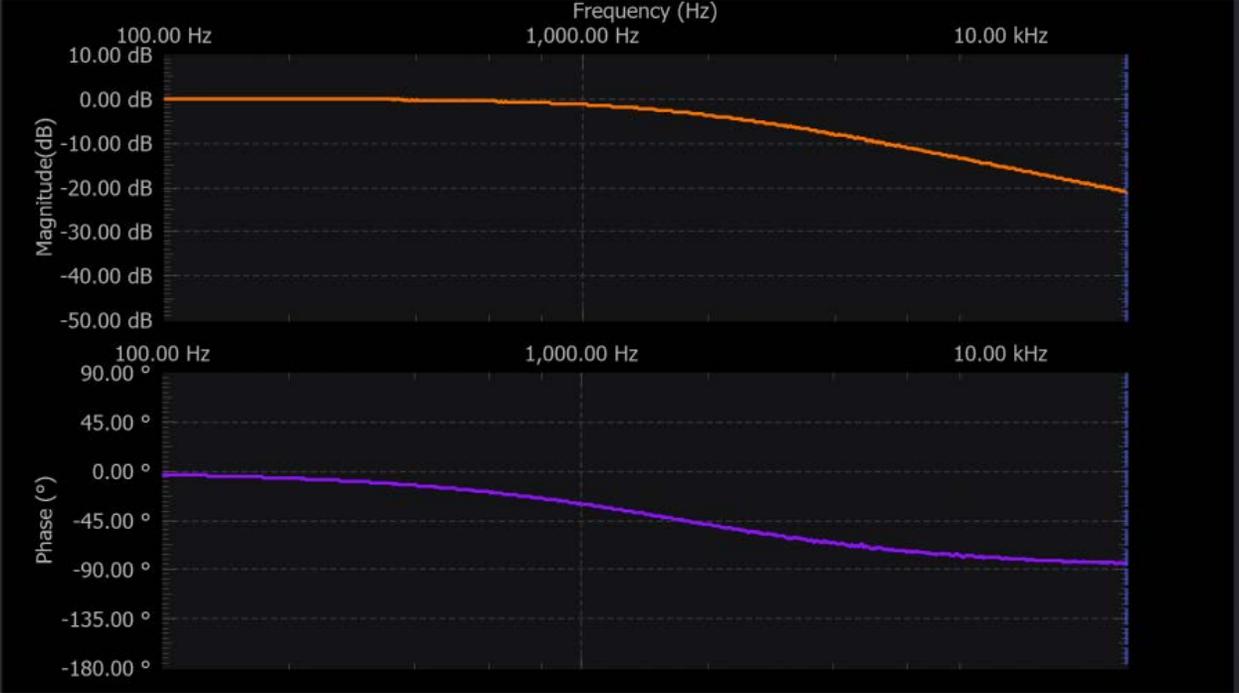


Figure 5. First-Order RC Filter Frequency Response.

## Second-Order RC Filter

### Hardware Setup

Add a second RC low-pass section to the previous filter as shown in Figure 6.

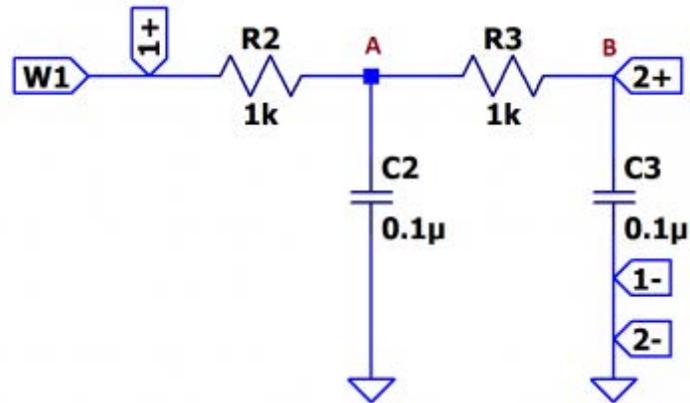


Figure 6. Second-Order RC Filter.

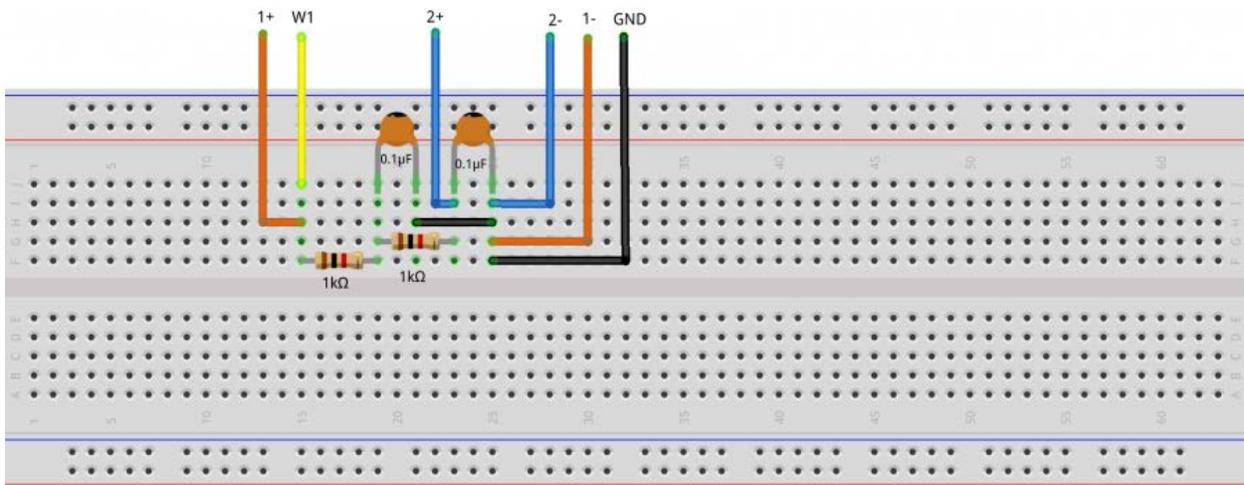


Figure 7. Second-Order RC Filter Breadboard Layout.

### Procedure

Keep the same settings on the Network Analyzer. Connect Oscilloscope channel 2 after the first RC stage (at node A) and do a single sweep. This will be the reference sweep and can be kept on the plot by pressing the Snapshot button in the Reference section of the Network Analyzer General Settings. Move the Oscilloscope channel 2 to node B (after the second RC stage) and do another sweep. You should now see the frequency response after both RC stages as in Figure 8.

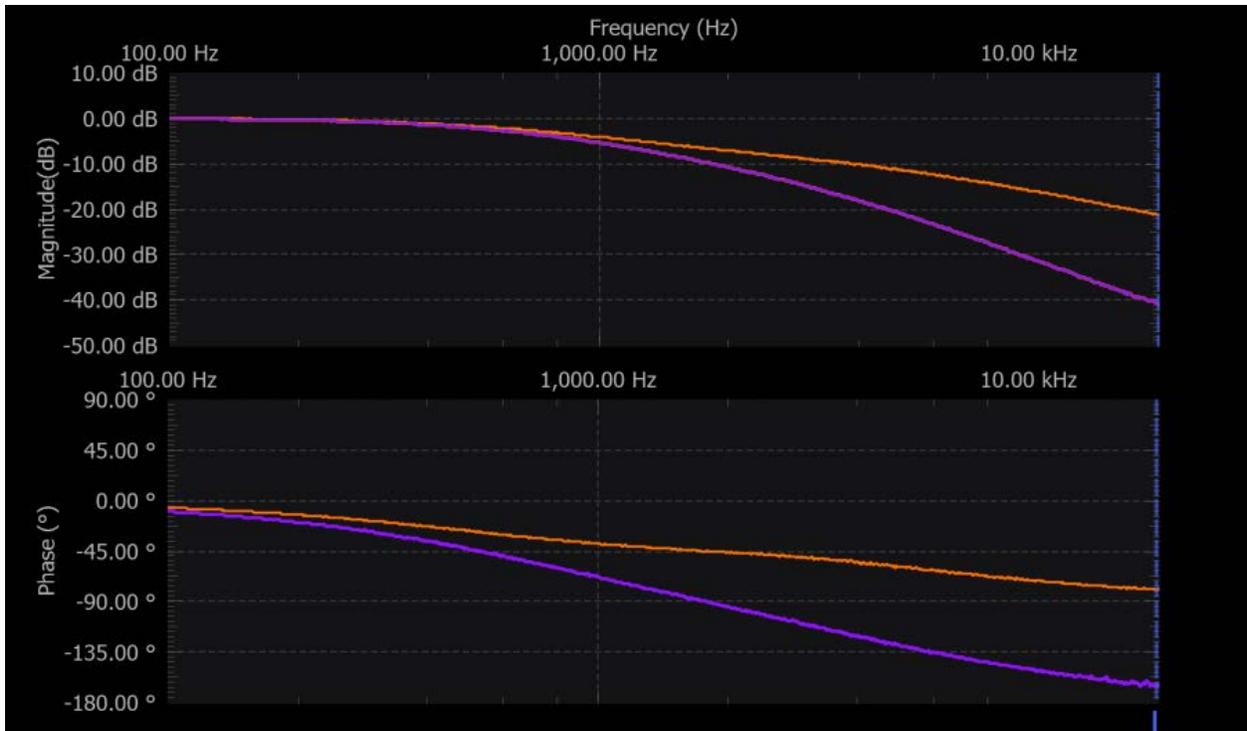


Figure 8. Second-Order RC Filter Frequency Response.

## Third-Order RC Filter

### Hardware Setup

As a further extension, add a third RC section to make a third-order filter as shown in Figure 9.

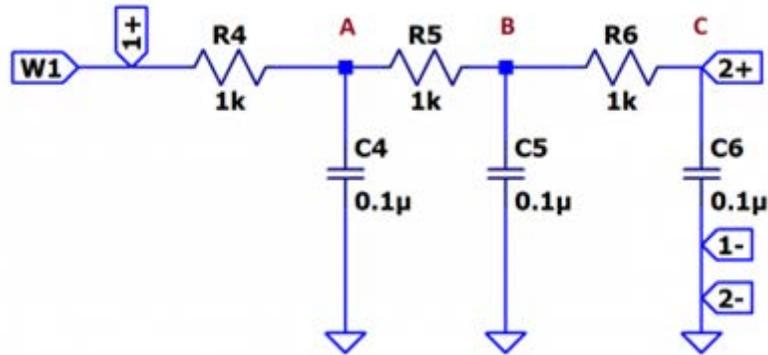


Figure 9. Third-Order RC Filter.

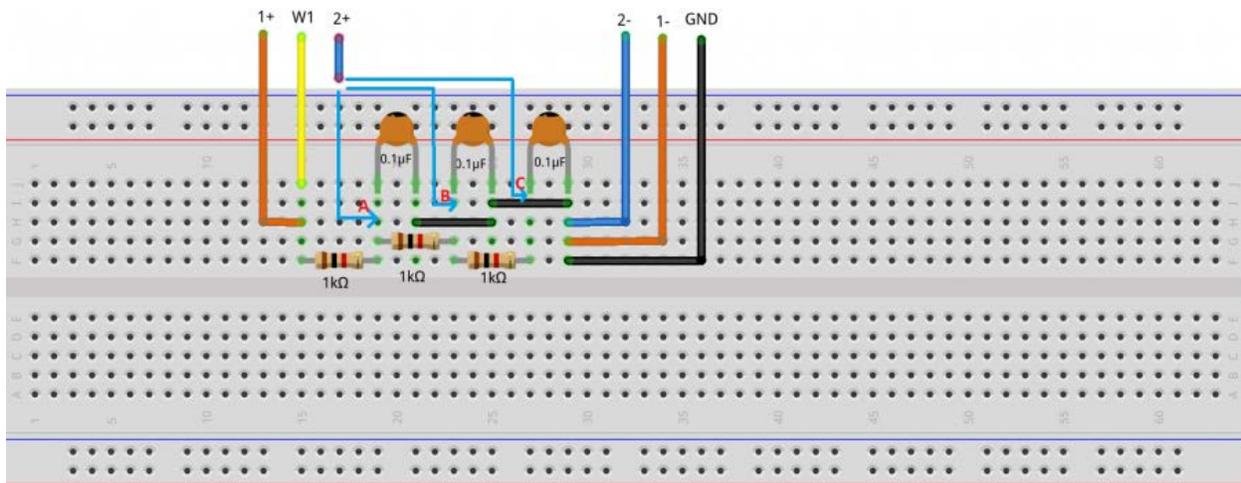


Figure 10. Third-Order RC Filter Breadboard Layout.

### Procedure

Keep the same settings on the Network Analyzer. Connect Oscilloscope channel 2 after the first RC stage (point A shown in Figure 9) and do a single sweep. This will be the reference sweep and can be kept on the plot by pressing the Snapshot button in the Reference section of the Network Analyzer General Settings. Move the Oscilloscope channel 2 to point B (after the second RC stage) and do another sweep and press the Snapshot button. You should now see the frequency response after both RC stages. To obtain the frequency response of the third stage move Oscilloscope channel 2 to point C and do another sweep. You should now see all three responses as shown in Figure 11.

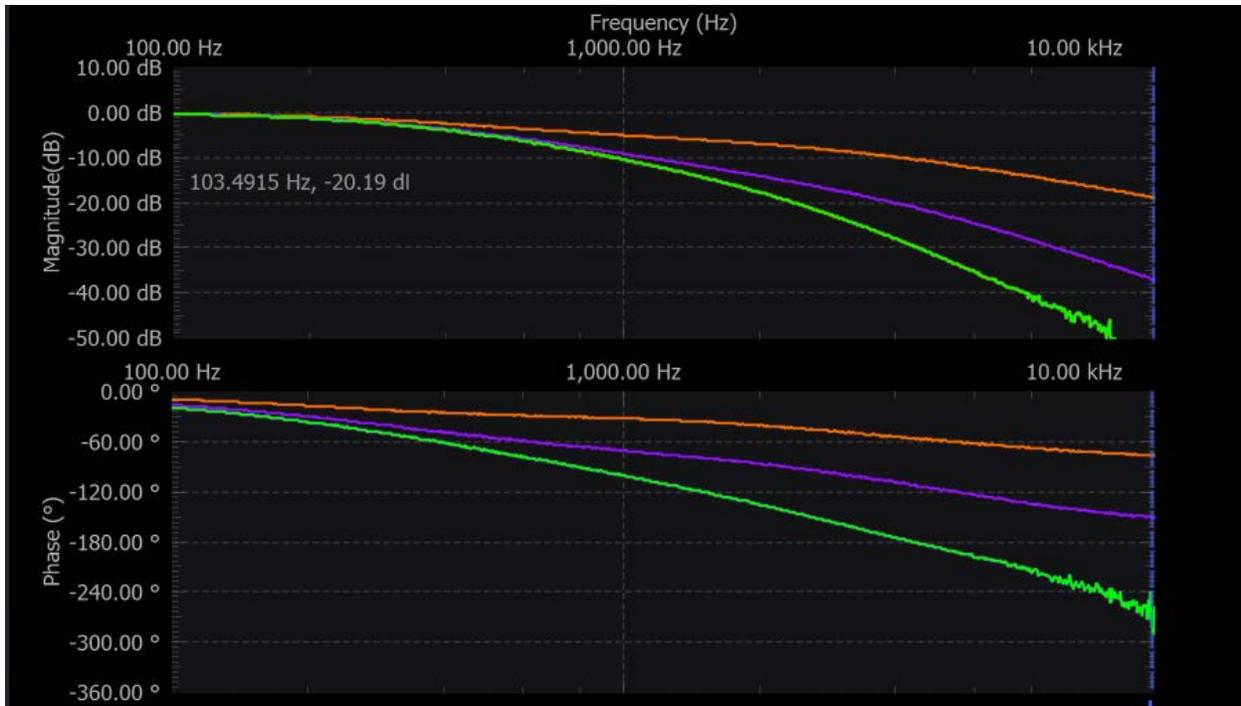


Figure 11. Third-Order RC Filter Frequency Response.

Change the components to  $R4 = 1 \text{ k}\Omega$ ,  $R5 = 10 \text{ k}\Omega$ ,  $R6 = 100 \text{ k}\Omega$  and  $C4 = 0.1 \text{ }\mu\text{F}$ ,  $C5 = 0.01 \text{ }\mu\text{F}$ ,  $C6 = 0.001 \text{ }\mu\text{F}$ . Repeat the same steps to plot the frequency response for this new cascaded filter.

### Questions/Review:

1. What are the differences between the plots for the second-order filter? (One plot was obtained with 2+ at point A and the other with 2+ at point B).
2. What are the differences between the plots for the third-order filter? (The plots were obtained by the same procedure, the third one being obtained with 2+ at point C).
3. How do your measured results compare to your simulation results (as in Figure 2)? Explain any differences.

### Report:

Your report should include, at a minimum, screen captures of the Network Analyzer/Oscilloscope displays you obtain, and meaningful discussion and interpretation of your results. It should be assembled in a reasonable report form, not just a collection of pictures. Pretend like you're writing a report for your project manager to explain to her/him what you did and what you think you learned.

Please also include any comments or suggestions you feel may help to improve this experiment for future students.