

Homework Problem #004

The portion of the circuit enclosed by the dashed box converts a voltage source into a current source driving a grounded load. Show that regardless of the value of R_L , the output current is

$$I_{out} = V_S / R_1.$$

