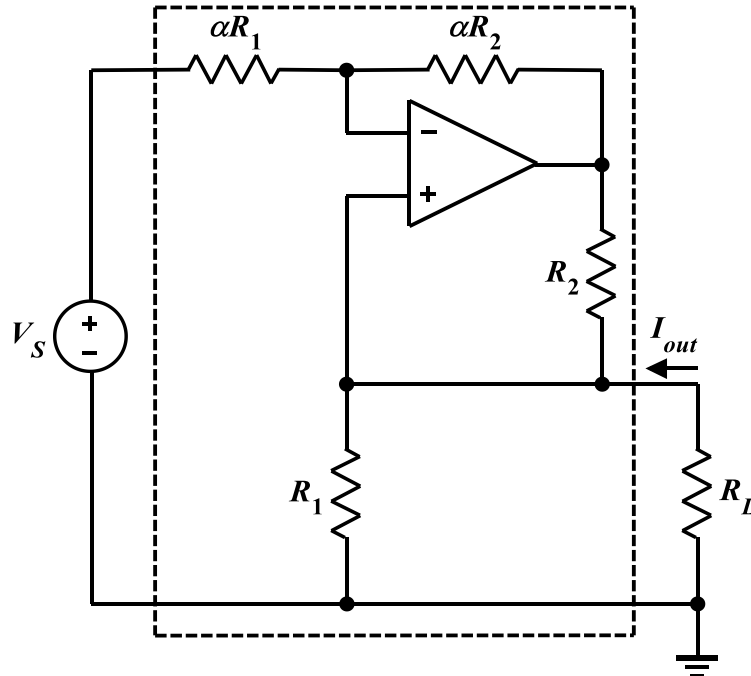


Homework Problem #005

Using the circuit from Homework Problem #004 (copied above), design a voltage-to-current converter to meet the following requirements:

- $V_S = 5 \text{ V}$.
- $I_{out} = 10 \text{ mA}$ when the load resistance R_L varies from $100 \text{ } \Omega$ to $500 \text{ } \Omega$.
- The current drawn from the source V_S is no larger than 0.5 mA .
- The op amp output voltage is no larger than its saturation value of $V_{sat} = 20 \text{ V}$.