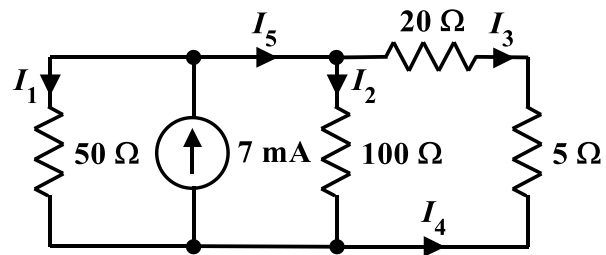


EE 4474/5574
Homework Problem #006



(a) Determine the value of I_1 .

(b) Determine the value of I_2 .

(c) Determine the value of I_3 .

(d) Determine the value of I_4 .

(e) Determine the value of I_5 .