

Homework Problem #12

Determine the impedance parameters (z parameters) of the two-port network shown below. Be sure to specify the units and proper sign for each parameter.

