

**Homework Problem #16**

Determine the hybrid parameters (h parameters) of the two-port network shown below. Be sure to specify the units and proper sign for each parameter.

