

Homework Problem #17

Determine the inverse hybrid parameters (g parameters) of the two-port network shown below. Be sure to specify the units and proper sign for each parameter.

