

Homework Problem #18

Determine the admittance parameters (y parameters) of the two-port network shown below. Be sure to specify the units and proper sign for each parameter.

